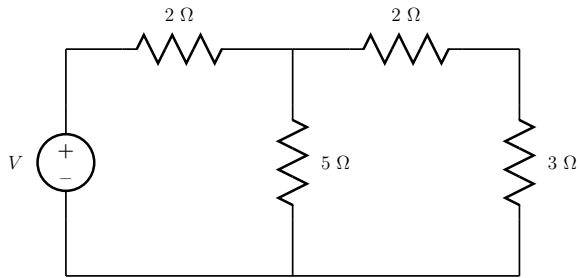



Preparation for Circuits

Concept Review


1. The power absorbed by the $5\ \Omega$ resistor is $20\ \text{W}$. Find V .



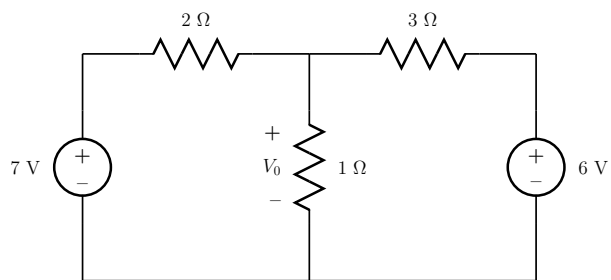
2. Use the node-voltage or loop-current method to find V_0 .



3. Find V_X .

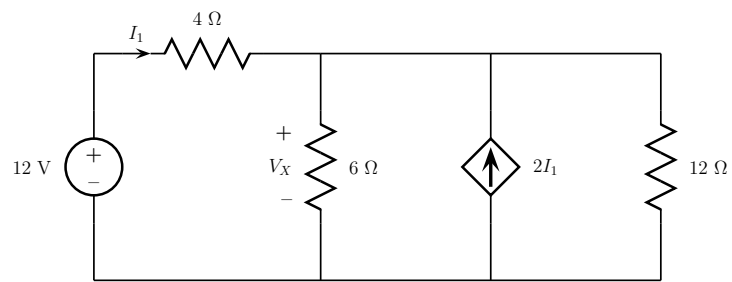

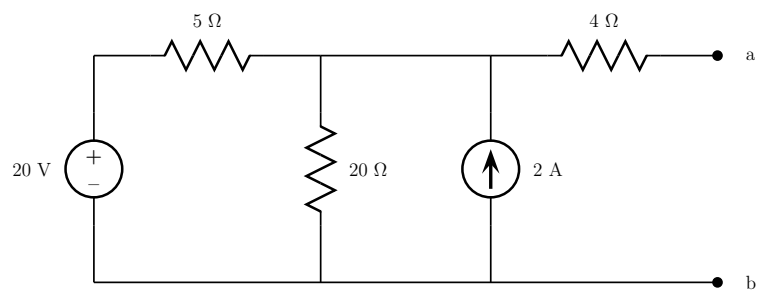4. Find the Thevenin equivalent at the terminals a and b .



5. Use superposition to find V . Check your work with source transformations.

