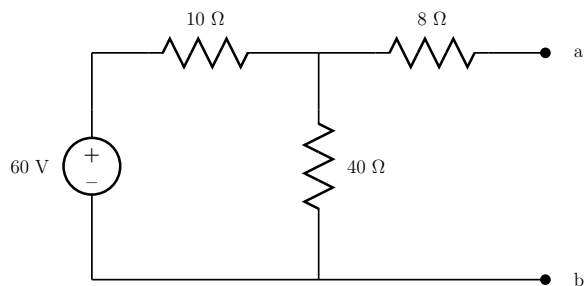



Preparation for Circuits

Concept Questions: Thevenin and Norton Equivalent Circuits


1. Find the Thevenin equivalent circuit at terminals a and b :



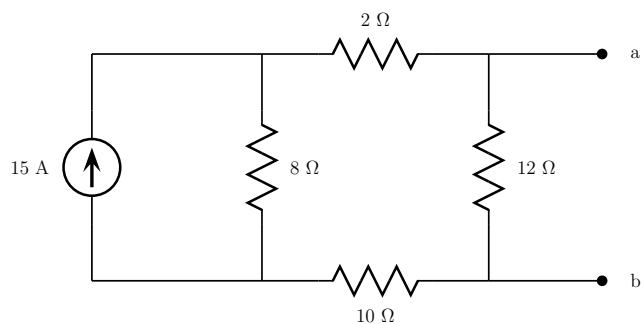2. Find the Thevenin and Norton equivalent circuits at terminals a and b :



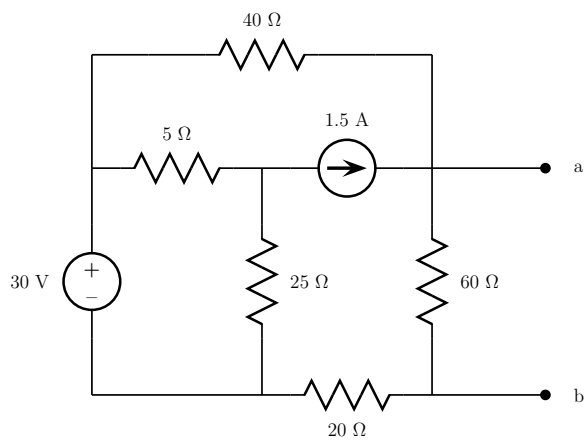3. Find the Thevenin and Norton equivalent circuits at terminals a and b :



4. Find the Thevenin equivalent circuit at terminals a and b :

