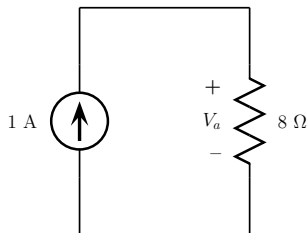


## Preparation for Circuits

### Concept Questions: Ohm's Law and the Passive Sign Convention


---

1. Calculate  $V_a$ :




2. What is the power dissipated by the resistor in the previous problem?

3. Calculate  $I_b$ :

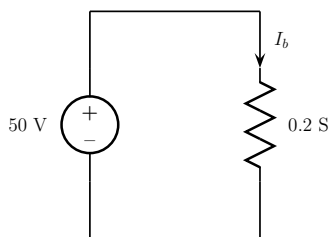


4. What is the power dissipated by the resistor in the previous problem?

5. Calculate  $V_c$ :

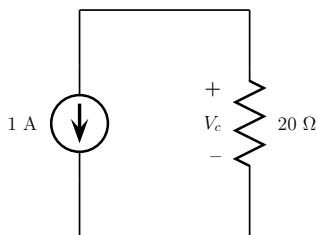


6. What is the power dissipated by the resistor in the previous problem?

7. Calculate  $I_d$ :

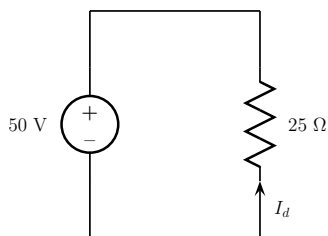


8. What is the power dissipated by the resistor in the previous problem?:

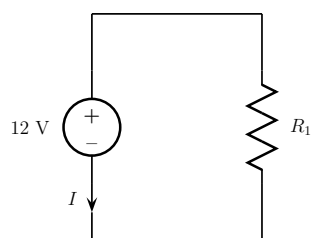9. What is  $I$  if  $R_1 = 40\text{ k}\Omega$ ?




- (A) 4.8 mA
- (B) -4.8 mA
- (C) 0.3 mA
- (D) -0.3 mA

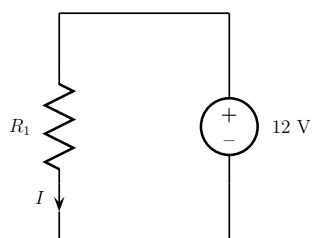10. What is  $I$  if  $R_1 = 40\text{ k}\Omega$ ?




- (A) 0.3 mA
- (B) -4.8 mA
- (C) -0.3 mA
- (D) 4.8 mA

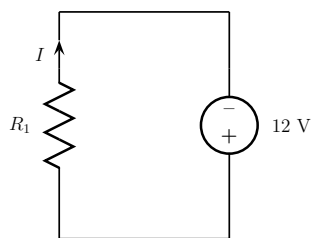11. What is  $I$  if  $R_1 = 40\text{ k}\Omega$ ?




- (A) -4.8 mA
- (B) -0.3 mA
- (C) 0.3 mA
- (D) 4.8 mA

12. What are  $I$  and  $V$ ?

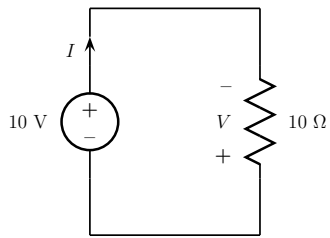

- (A) -1A, 10V
- (B) 1A, -10V
- (C) -1A, -10V
- (D) 1A, 10V

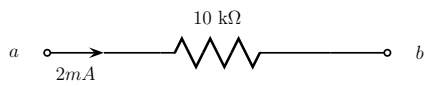13. What is the voltage across the resistor?



- (A) 5 V, + @  $a$ , - @  $b$
- (B) 20 V, - @  $a$ , + @  $b$
- (C) 20 V, + @  $a$ , - @  $b$
- (D) 5 V, - @  $a$ , + @  $b$