

Electrical Engineering (Circuits)

Power

1. A current $10,000 \mu\text{A}$ can be felt by humans. How many milliamps (mA) is this?

- (A) 10.0 (C) 100.0
(B) 1.0 (D) 0.1


2. A voltage of 10 MV is equal to:

- (A) 10,000 GV (C) 0.001 GV
(B) 0.01 GV (D) 1,000 GV

3. 10^{-2} seconds is equal to:


- (A) 10 ms (C) 1 ms
(B) 10^2 ms (D) 0.1 ms

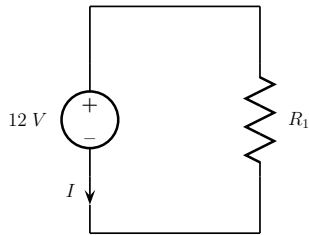4. What is I if $R_1 = 40 \text{ k}\Omega$?




- (A) -0.3 mA (C) -4.8 mA
(B) 4.8 mA (D) 0.3 mA

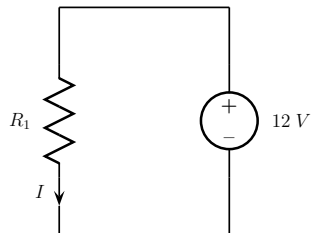5. What is I if $R_1 = 40 \text{ k}\Omega$?



- (A) 0.3 mA (C) -4.8 mA
(B) -0.3 mA (D) 4.8 mA

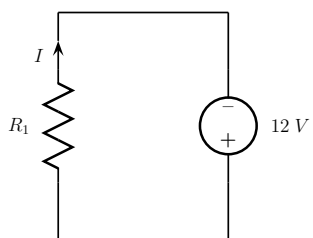6. What is I if $R_1 = 40 \text{ k}\Omega$?




(A) -0.3 mA

(C) 4.8 mA

(B) -4.8 mA

(D) 0.3 mA

7. What are I and V ?

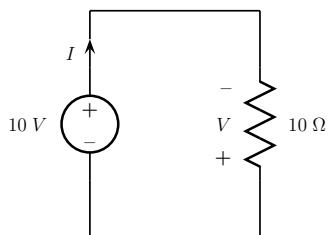


(A) $-1\text{A}, -10\text{V}$

(C) $1\text{A}, -10\text{V}$

(B) $1\text{A}, 10\text{V}$

(D) $-1\text{A}, 10\text{V}$

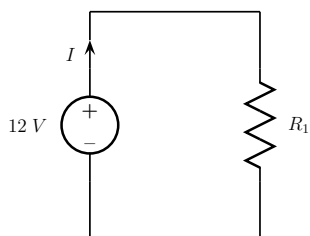8. What is the power absorbed by R_1 if $R_1 = 10 \text{ k}\Omega$?




(A) -14.4 mW

(C) 14.4 mW

(B) -12.2 mW

(D) 12.2 mW

9. What is V_S if $I = 2\text{A}$?

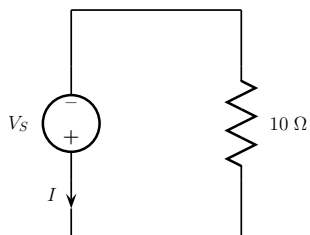


(A) -20 V

(C) -5 V

(B) 5 V

(D) 20 V

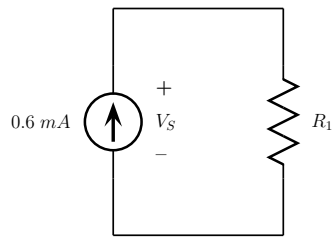
10. What is V_S if $R_1 = 10\text{ k}\Omega$?



- (A) 6 V
(B) -0.6 V
(C) -6 V
(D) 0.6 V


11. **T** or **F**: According to the *passive sign convention*, a positive power is associated with a component that is absorbing energy.

12. What is V_0 ?

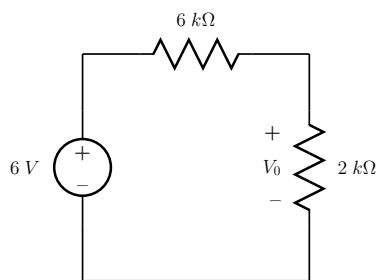


- (A) $\frac{3}{2}\text{ V}$
(B) $\frac{3}{4}\text{ V}$
(C) 2.5 V
(D) 4.5 V

13. What are V_1 and V_2 ?

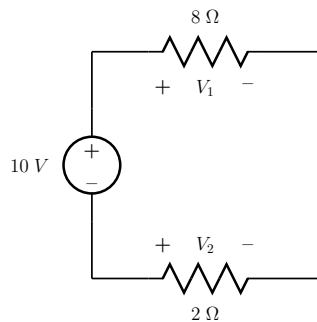

- (A) 8V, -2V
(B) 8V, 2V
(C) -8V, 2V
(D) -8V, -2V

14. What are V_1 and V_2 ?

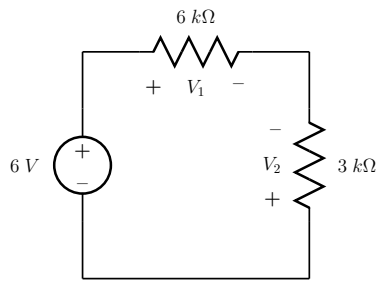


(A) 6V, 2V

(C) 4V, 2V

(B) 4V, -2V

(D) -6V, 2V

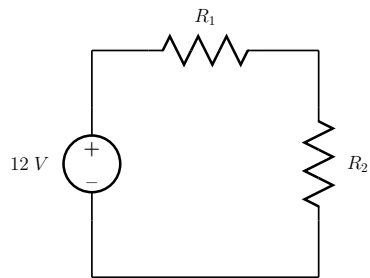15. If the power supplied by the voltage source is 60 W, how much power is dissipated by R_1 if $R_2 = 1 \Omega$?




(A) 35 W

(C) 55 W

(B) 45 W

(D) 25 W

16. What is I_1 ?

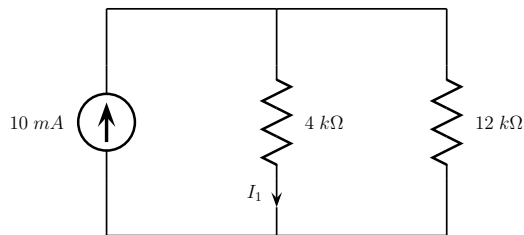


(A) 7.5 mA

(C) 10 mA

(B) 5 mA

(D) 2.5 mA

17. What are I_1 and I_2 ?

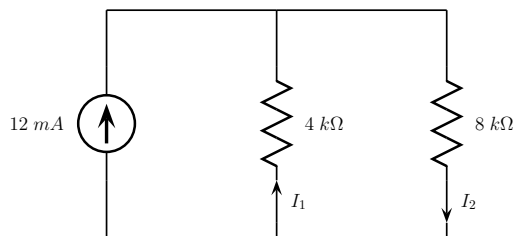


(A) -4 mA, 8 mA

(C) 4 mA, 8 mA

(B) -8 mA, 4 mA


(D) -8 mA, 4 mA

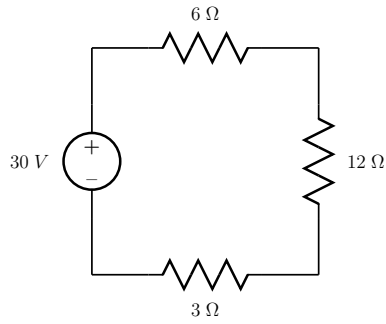18. What is R_{EQ} for the three resistors?




- (A) 19 Ω (C) 9 Ω
 (B) 21 Ω (D) 18 Ω

19. What is V_3 ?

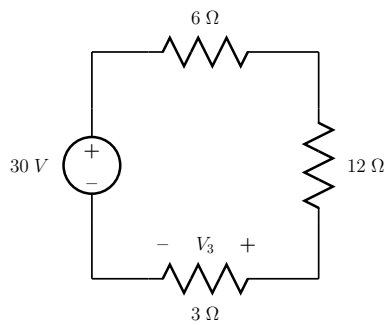


- (A) $-\frac{30}{7}$ V (C) $\frac{10}{7}$ V
 (B) $\frac{30}{7}$ V (D) $-\frac{10}{7}$ V

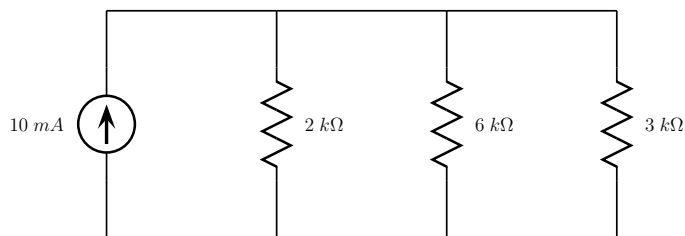20. What is R_{EQ} for the three resistors below?




- (A) $\frac{36}{11}$ kΩ (C) 1 kΩ
 (B) 11 kΩ (D) $\frac{11}{36}$ kΩ

21. What is I_2 ?

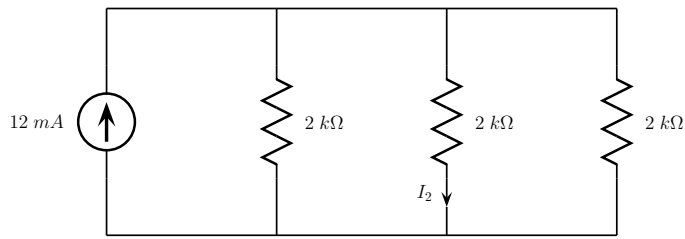

- (A) 2 mA (C) 6 mA
(B) 8 mA (D) 4 mA

22. What is R_{ab} ?

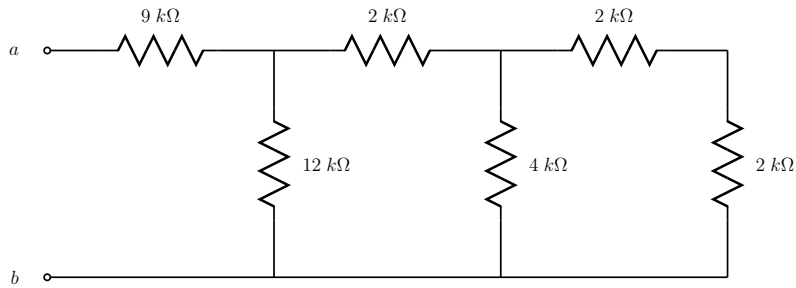

- (A) $6\text{ k}\Omega$ (C) $9\text{ k}\Omega$
(B) $15\text{ k}\Omega$ (D) $12\text{ k}\Omega$


23. What resistor value would need to be added, in series, to two parallel $10\text{ }\Omega$ resistors to make an overall resistance of $15\text{ }\Omega$?

- (A) $25\text{ }\Omega$ (C) $7.5\text{ }\Omega$
(B) $10\text{ }\Omega$ (D) $5\text{ }\Omega$

24. **T** or **F**: Three resistors in series will have a larger overall resistance than any of the individual resistors.


25. **T** or **F**: Three resistors in parallel will have a larger overall resistance than any of the individual resistors.

26. Find R_{ab} .

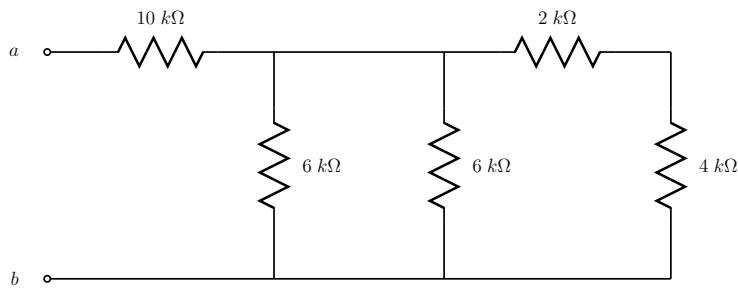

- (A) $15\text{ k}\Omega$ (C) $12\text{ k}\Omega$
(B) $9\text{ k}\Omega$ (D) $6\text{ k}\Omega$

27. What is I_1 ?

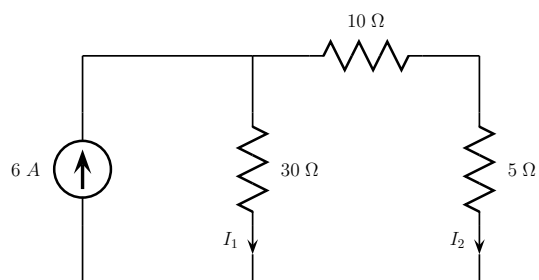


(A) 4 A

(B) 8 A

(C) 6 A

(D) 2 A

28. What is I_2 ?

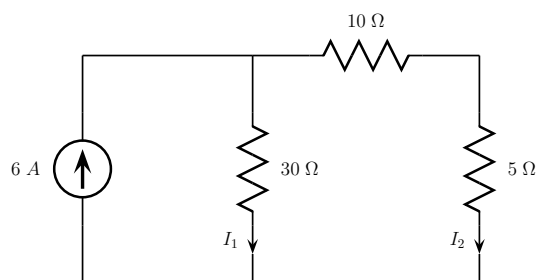


(A) 2 A

(B) 8 A

(C) 6 A

(D) 4 A

29. What is V_1 ?

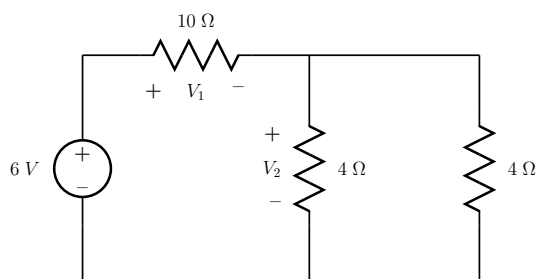


(A) 1 V

(B) 2 V

(C) 5 V

(D) 4 V

30. What is V_2 ?

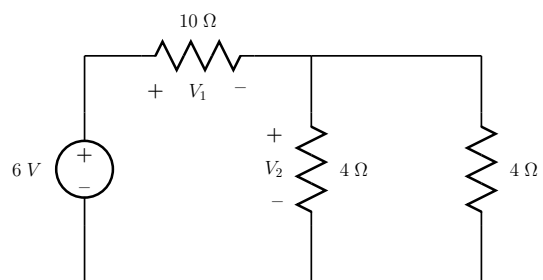

(A) 2 V

(B) 4 V

(C) 1 V

(D) 5 V