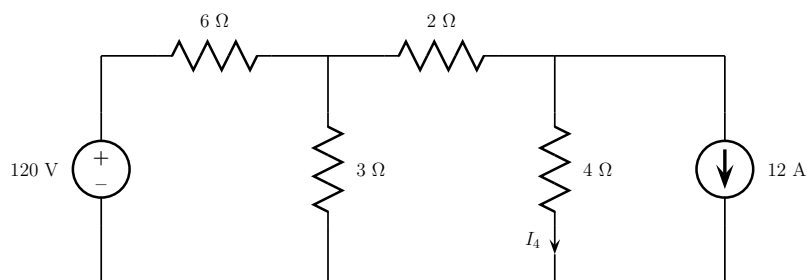



Preparation for Circuits

Concept Questions: Superposition


1. Find I_4 .



2. Find V .

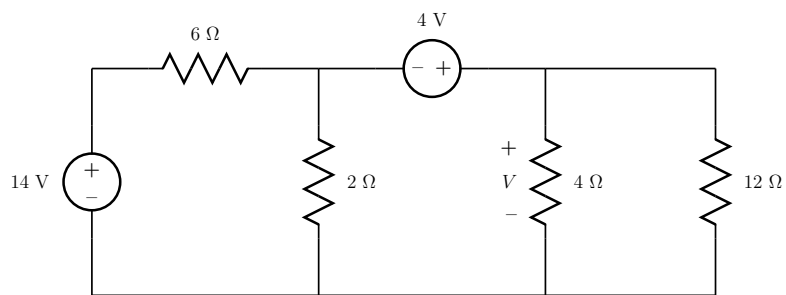

3. Find V .

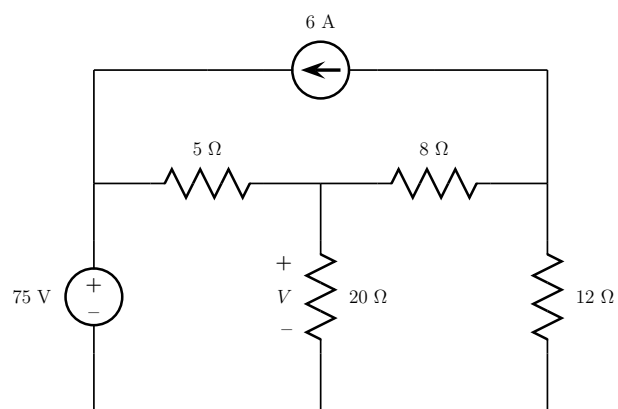

4. Find V_0 .

