

Preparation for Circuits


Concept Questions: The Node-Voltage Method

In nodal analysis, the following 4 steps should be followed:


- (1) Label all nodes (label one of them as the reference)
- (2) Define currents in each resistive branch
- (3) Write KCL only at non-reference nodes nodes with no voltage sources present
- (4) Express all currents in terms of node voltages ($I = \frac{V}{R}$)
- (5) Solve for unknown node voltages

The **goal** is to find all **node voltages** - the voltage from a specific node to the reference node.


1. What is I_s and V_2 ?

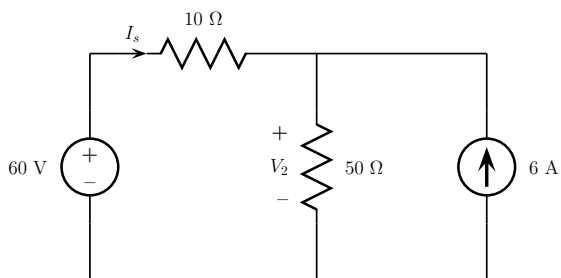

2. Find V_1 , V_2 , and I_1 .

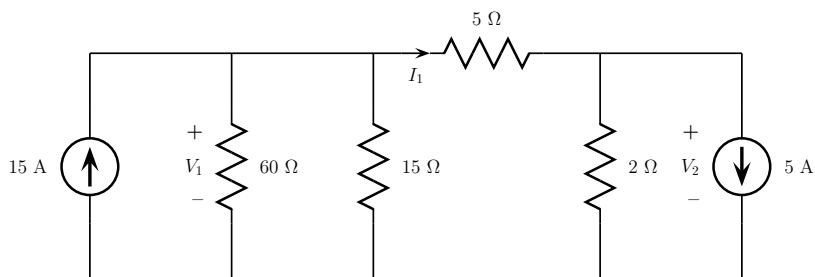

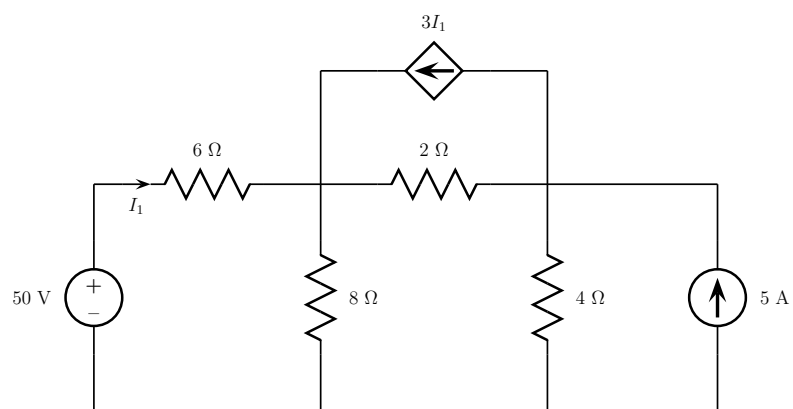3. Find the power associated with each source.



4. Find I_0 .

